We started by creating two open circuits.
Circuit consisted of:
1. Output: LED
2. Power/Force: Cell
3. Connectiong components: Copper wire, copper tape, jumper wire
4. Control: Conductor (copper wire)
Mechanism: When the two bands, with individual open circuits, get pressed against each other they light up (LED). Each band completes the open circuit of the other.

Iteration 1- we used copper wire to make a circuit but the weight distrabution made it difficult to wear.
iteration 2- we used copper tape to create a circuit on a paper band then taped a lithuim battery and led bulb to it. This kept the weight distrabution better. The two bracelets would join to create a closed circuit lighting up the led bulbs into red hearts.
iteration 3. We created a single closed circuit with a reed switch. the other bracelet contained a magnet so that when in proximity the led would light up.

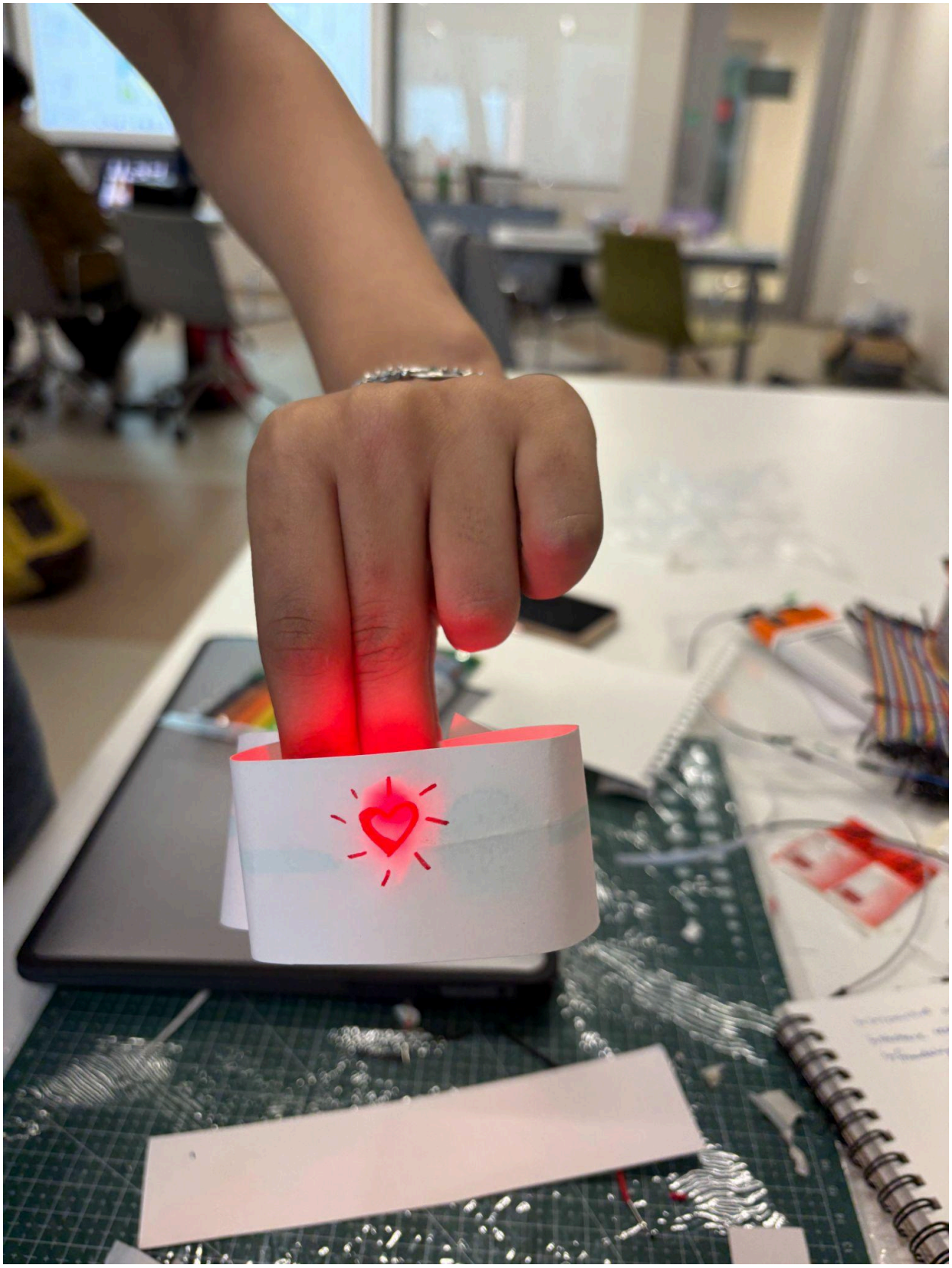

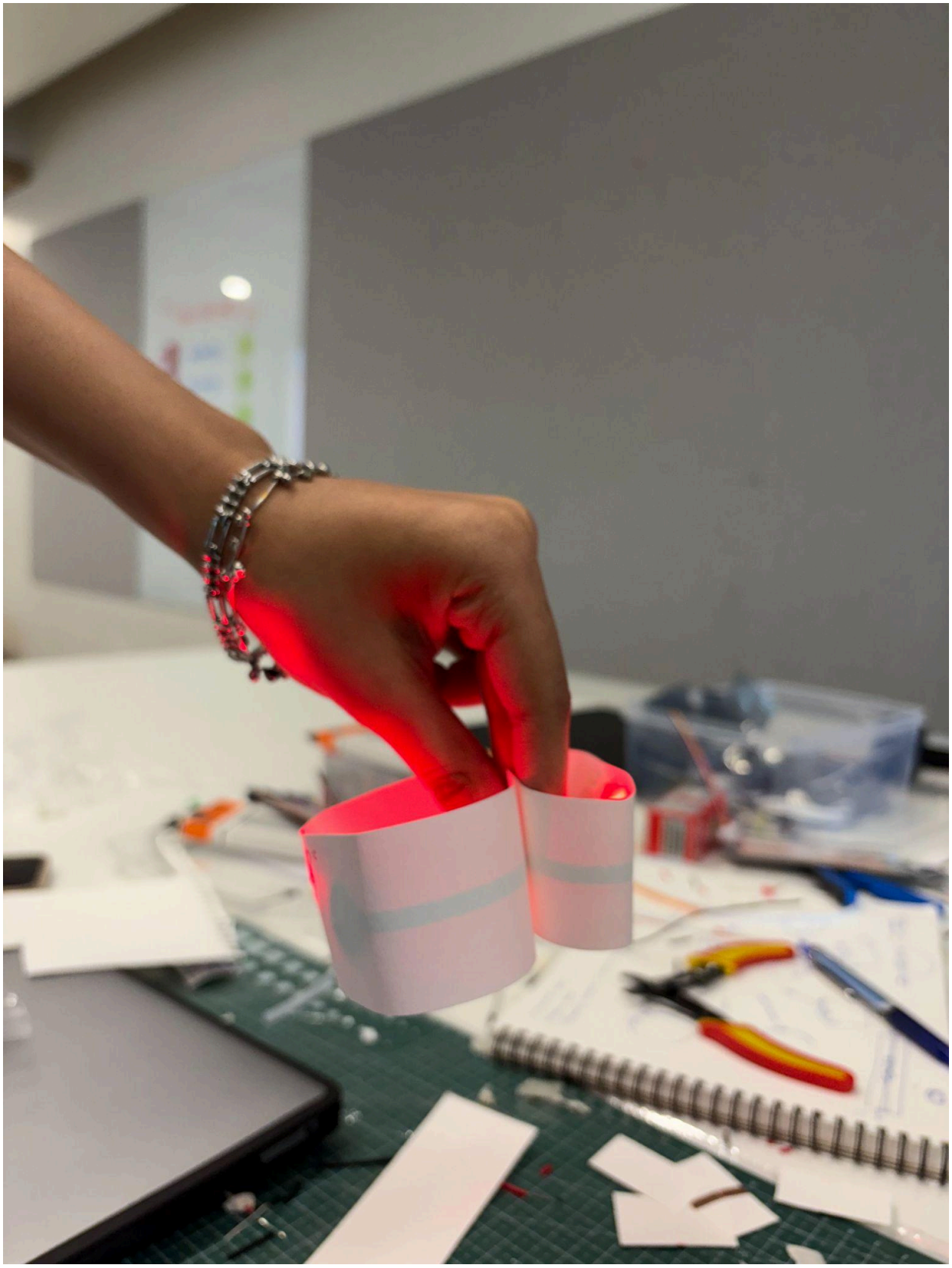

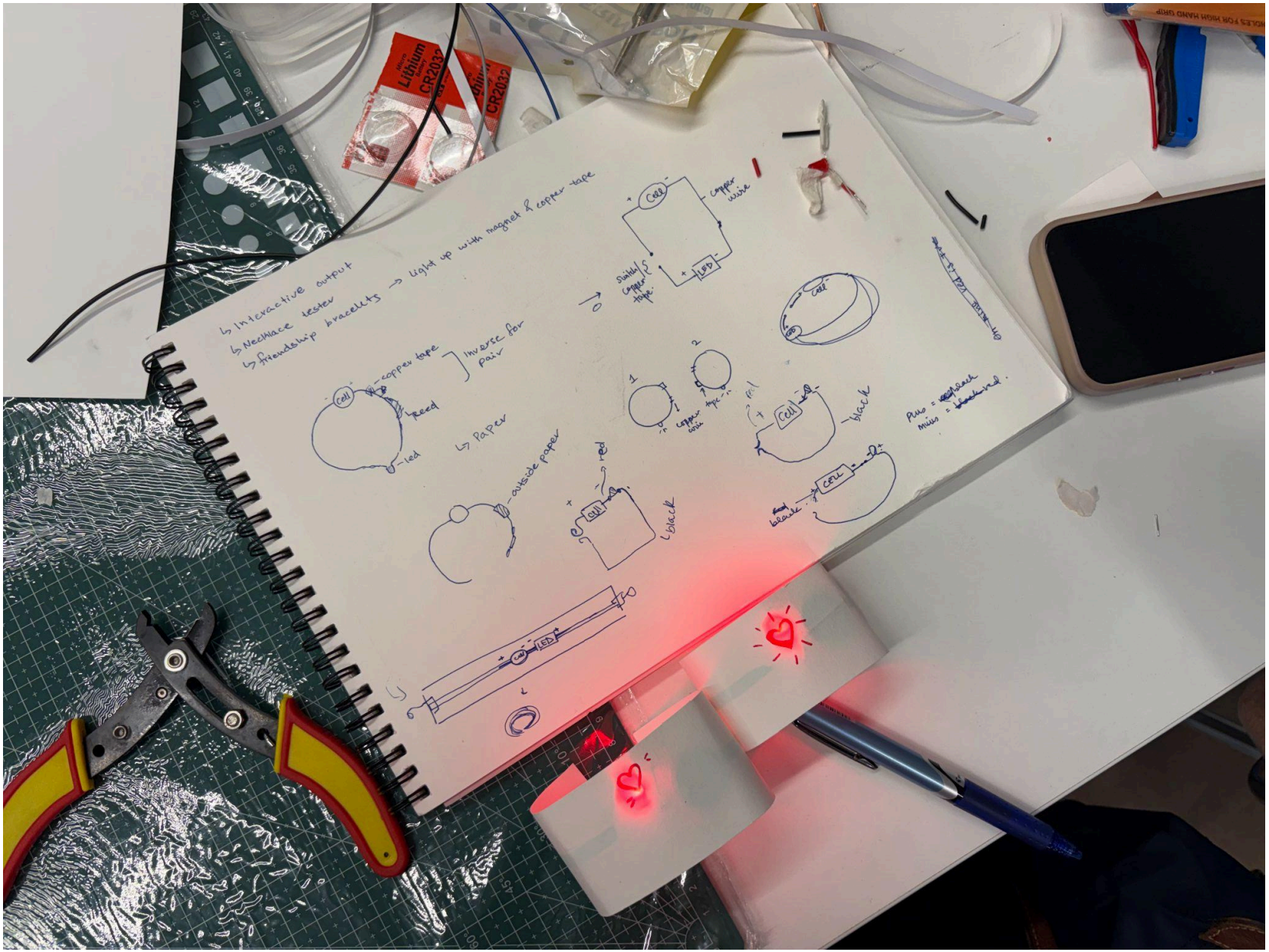
Lithium
CR2032
CR2032
↳ Interactive output
↳ Necklace tester
↳ friendship bracelets → light up with magnet & copper tape
copper tape
Inverse for pair
cell
reed
led
↳ Paper
outside paper
red
black
cell
LED
copper wire
Stable copper tape
copper wire
cell
LED
cell
black
cell
brass
Pins = black
Wire = bendable.

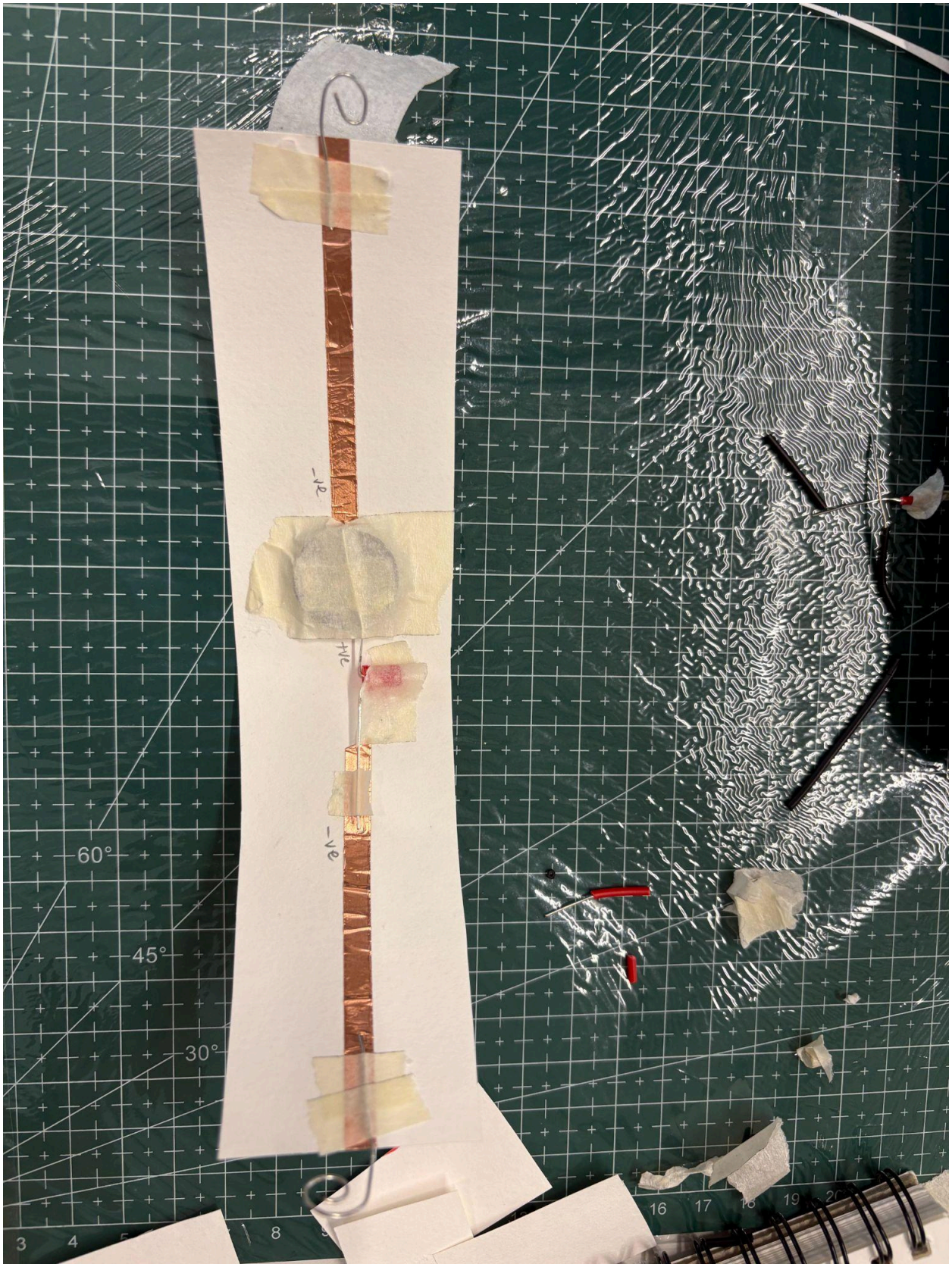
-ve
+ve
-ve
60°
45°
30°